

# Lab Assignment 1

TEAM MEMBERS:

Shiva Ghose, @gshiva

John Peterson, @jrpeters

Wenjian Bai, @baiwenji

## Question 1

## Question 2

a

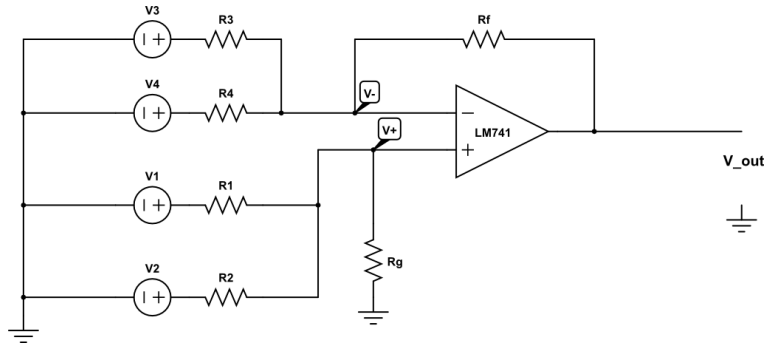


Figure 1: The required circuit diagram for question 2.

b

Circuit analysis:

At the non-inverting terminal, we effectively have a circuit represented by figure 2. We can use Kirchoff's voltage law along with the superposition theorem, we see:

Voltage at  $V^+$  due to  $V_1$ ,  $V_1^+$ , is given by:

$$V_1^+ = \frac{\frac{R_2 R_g}{R_2 + R_g}}{R_1 + \frac{R_2 R_g}{R_2 + R_g}} V_1$$

$$\therefore V_1^+ = \left( \frac{1}{\frac{R_1}{R_g} + \frac{R_1}{R_2} + 1} \right) V_1$$

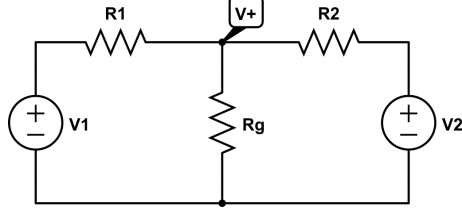


Figure 2: Equivalent circuit at the non-inverting terminal

Similarly, voltage at  $V^+$  due to  $V_2$ ,  $V_2^+$ , is given by:

$$V_2^+ = \frac{\frac{R_1 R_g}{R_1 + R_g}}{R_2 + \frac{R_1 R_g}{R_1 + R_g}} V_2$$

$$\therefore V_2^+ = \frac{1}{\frac{R_2}{R_g} + \frac{R_2}{R_1} + 1} V_2$$

Using the superposition theorem to recombine the values, we find that  $V^+$  is given by:

$$V^+ = V_1^+ + V_2^+$$

$$V^+ = \frac{1}{\frac{R_1}{R_g} + \frac{R_1}{R_2} + 1} V_1 + \frac{1}{\frac{R_2}{R_g} + \frac{R_2}{R_1} + 1} V_2$$

We can now move on to the inverting terminal of the op-amp. The corresponding equivalent circuit is shown in figure 3. Analyzing this circuit, we see that:

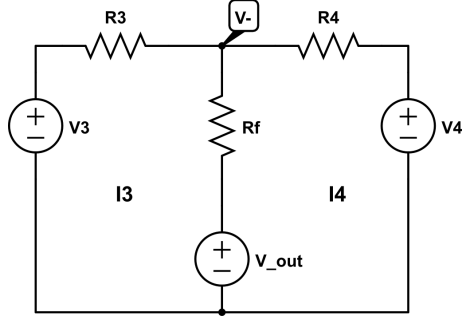


Figure 3: Equivalent circuit at the non-inverting terminal

$$I_3 R_3 = V_3 - V^-$$

$$I_4 R_4 = V_4 - V^-$$

$$V^- - V_{out} = (I_3 + I_4) R_f$$

Substituting from the above equations, we get:

$$V^- - V_{out} = \left( \frac{V_3 - V^-}{R_3} + \frac{V_4 - V^-}{R_4} \right) R_f$$

Reordering the terms, we get:

$$V_{out} = V^- - \left( \frac{V_3 - V^-}{R_3} + \frac{V_4 - V^-}{R_4} \right) R_f$$

$$\Rightarrow V_{out} = V^- \left( \frac{R_f}{R_3} + \frac{R_f}{R_4} + 1 \right) - \left( \frac{R_f}{R_3} \right) V_3 - \left( \frac{R_f}{R_4} \right) V_4$$

We also know that for an ideal op-amp,  $V^+ = V^-$ , hence we get:

$$V_{out} = \left( \frac{R_f}{R_3} + \frac{R_f}{R_4} + 1 \right) \left( \frac{1}{\frac{R_1}{R_g} + \frac{R_1}{R_2} + 1} \right) V_1 + \left( \frac{R_f}{R_3} + \frac{R_f}{R_4} + 1 \right) \left( \frac{1}{\frac{R_2}{R_g} + \frac{R_2}{R_1} + 1} \right) V_2 - \left( \frac{R_f}{R_3} \right) V_3 - \left( \frac{R_f}{R_4} \right) V_4$$

This is equation is the mathematical representation of the required problem which was;  $V_{out} = a_1 V_1 + a_2 V_2 - a_3 V_3 - a_4 V_4$ , i.e. :

$$a_1 = \left( \frac{R_f}{R_3} + \frac{R_f}{R_4} + 1 \right) \left( \frac{1}{\frac{R_1}{R_g} + \frac{R_1}{R_2} + 1} \right)$$

$$a_2 = \left( \frac{R_f}{R_3} + \frac{R_f}{R_4} + 1 \right) \left( \frac{1}{\frac{R_2}{R_g} + \frac{R_2}{R_1} + 1} \right)$$

$$a_3 = \left( \frac{R_f}{R_3} \right)$$

$$a_4 = \left( \frac{R_f}{R_4} \right)$$

**c**